


SINGLE POLE OPAMP IN FEEDBACK

Note Title

12/21/2010

→ To see the bode plot of Amp, loop gain & Transfer function in 1 plot for comparison.

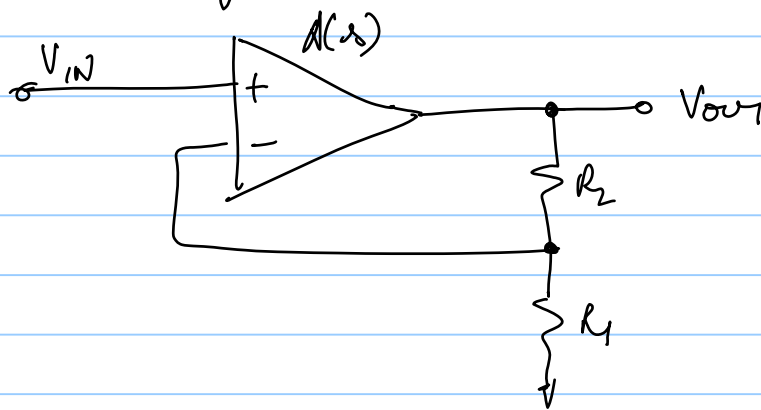
If we have a single pole block & we put it in feedback:



$$A(s) = \frac{A_0}{1 + \tau s}$$

pole = $-\frac{1}{\tau}$

The bode plot of $A(s)$ is:

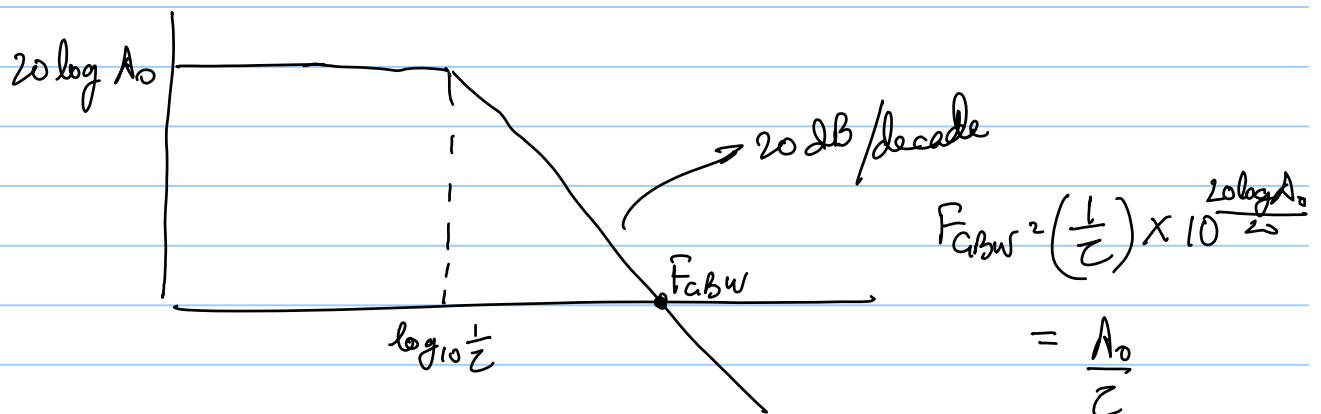


The loop gain of the above system which has to be considered to make the system stable is given as:

$$L.G. = A(s) \cdot \frac{R_1}{R_1 + R_2} = \frac{A(s)}{1 + R_2/R_1}$$

$$1 + \frac{R_2}{R_1} = G \text{ (Gain of ch)} = \frac{A_0/G}{(1 + \tau s)}$$

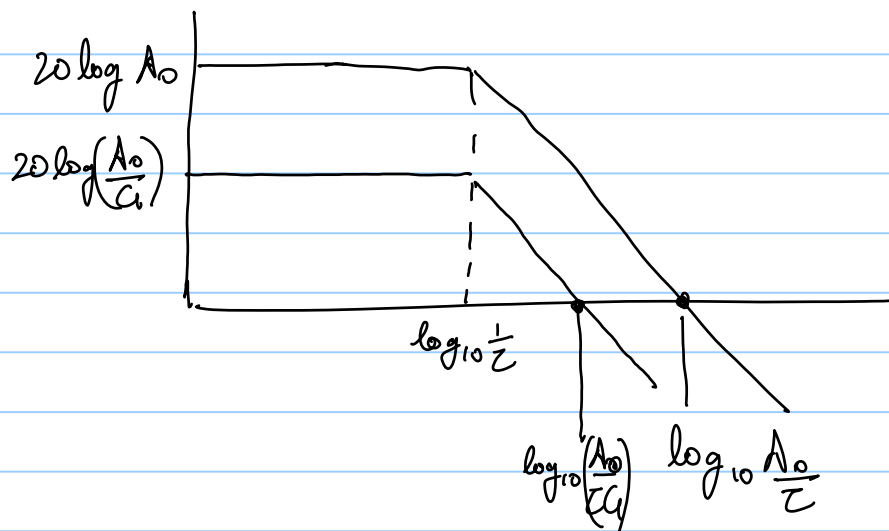∴ the bode plot showing the amplifier response & the loop gain is



→ Thus the loop gain has less DC gain & hence less Gain bandwidth.

→ Thus stabilizing it just got simpler compared to it in unity gain feedback.

The transfer function is given as :

$$\left(V_{IN} - V_{OUT} \frac{R_1}{R_1 + R_2} \right) A(s) = V_{OUT}$$

$$V_{IN} A(s) = V_{OUT} \left(\frac{A(s) R_1}{R_1 + R_2} + 1 \right)$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{A(s)}{1 + \frac{A(s)}{G}} = \frac{A_0}{(1 + s\tau) \left(1 + \frac{A_0}{(1 + s\tau)G} \right)}$$

$$TF = \frac{A_0}{1 + s\tau + \frac{A_0}{G}}$$

$$\text{Pole} = -\frac{1}{\tau} \left(1 + \frac{A_0}{G} \right)$$

$$\text{DC gain} = \frac{A_0}{1 + A_0/g}$$

Now to check if this point lies on any of the above 2 bode plots

The amplifier bode plot falling line equation is:

$$\frac{0 - 20 \log A_0}{\log \frac{1}{\omega} - \log \frac{1}{\omega_0}} = \frac{y - 20 \log A_0}{\log \omega - \log \frac{1}{\omega_0}}$$

$$\text{for } \omega = \frac{1}{\omega_0} \left(1 + \frac{A_0}{g}\right) \quad y = y_0$$

$$\Rightarrow \frac{-20 \log A_0}{\log \frac{1}{\omega_0} - \log \frac{1}{\omega_0}} = \frac{y_0 - 20 \log A_0}{\log \left(1 + \frac{A_0}{g}\right)}$$


$$-20 \log \left(1 + \frac{A_0}{g}\right) + 20 \log A_0 = y_0$$

$$y_0 = 20 \log \frac{A_0}{1 + A_0/g}$$

$$\therefore \text{Gain at that point is } \frac{A_0}{1 + A_0/g}$$

which is same as gain of transfer function at that frequency.

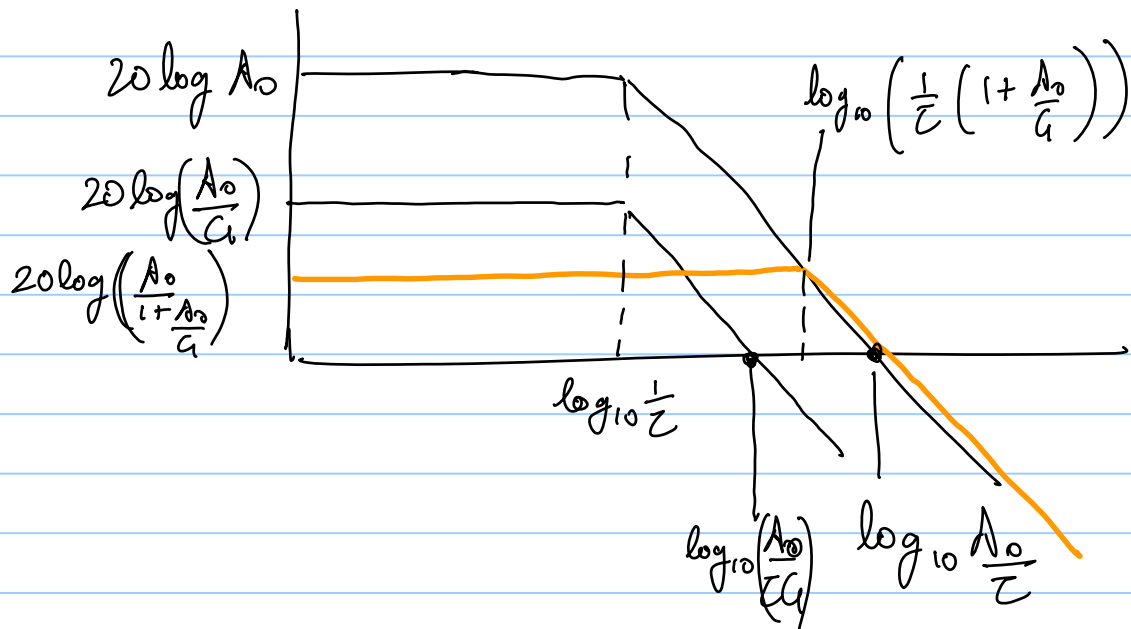Thus the bode plot with all 3 functions is:



Although we have to work to stabilize with pole at $\frac{1}{z}$ we get performance & bandwidth upto $\frac{1}{z} \left(1 + \frac{A_0}{a} \right) !!$

This is also obvious if you think that for a single pole system feedback does not change the F_{BW}